



Logic Gates & Boolean Algebra

The building blocks behind every digital circuit — and how to reason about them on paper


1. Boolean Algebra & Its Laws

Boolean algebra deals with variables that can only be 1 (true) or 0 (false). Every digital circuit — from a calculator to a laptop's processor — reduces its decisions to AND, OR, and NOT operations on 1s and 0s. The laws below let you simplify any such expression before wiring it into a circuit: fewer terms means fewer gates, which means smaller and cheaper hardware.

Law	AND form	OR form
Identity	$A \cdot 1 = A$	$A + 0 = A$
Null	$A \cdot 0 = 0$	$A + 1 = 1$
Idempotent	$A \cdot A = A$	$A + A = A$
Complement	$A \cdot A' = 0$	$A + A' = 1$
Commutative	$A \cdot B = B \cdot A$	$A + B = B + A$
Distributive	$A \cdot (B + C) = A \cdot B + A \cdot C$	$A + (B \cdot C) = (A + B) \cdot (A + C)$
Absorption	$A \cdot (A + B) = A$	$A + (A \cdot B) = A$
De Morgan's	$(A \cdot B)' = A' + B'$	$(A + B)' = A' \cdot B'$

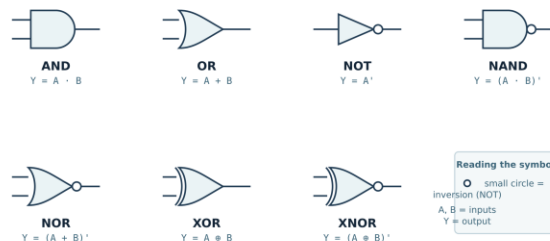2. Logic Gates — The Physical Form

Each Boolean operator has a matching gate symbol. Notice the pattern: NAND is AND with a bubble on the output, and NOR is OR with a bubble — that bubble always means "invert this signal."



3. Truth Tables & De Morgan's Theorem

A truth table lists every input combination and the resulting output. For two inputs there are always four rows (2^2):

A	B	AND (A·B)	OR (A+B)	XOR (A⊕B)
0	0	0	0	0
0	1	0	1	1
1	0	0	1	1
1	1	1	1	0

De Morgan's laws let you push a NOT through a bracket by flipping the operator inside: $(A \cdot B)' = A' + B'$, and $(A + B)' = A' \cdot B'$. In short — break the bracket, flip AND to OR (or OR to AND).

Dr. N.G.Thangamma

Assistant Professor, PG Department of Computer Science

St.Joseph's College (Arts & Science)